

Discussion #2 Problems and Solutions  
CSM51A / EEM16 Spring 2016  
April 8, 2016

Problems labeled with Textbook tags are taken from the class textbook (Dally & Harting).

**[Textbook 3.13] Dual Functions, I**

Find the dual of the following function and write it in normal form:  $f(x, y) = (x \wedge \bar{y}) \vee (\bar{x} \wedge y)$ .

---

**Solution:**

**[Textbook 3.17] Normal Form, II**

Rewrite the following Boolean expression in normal form:  $f(x, y, z) = x$ .

---

**Solution:**

**[Textbook 3.20] Equation from Schematic, I**

Write down a simplified Boolean expression for the functions computed by the logic circuit of Figure 1.

 


Figure 1: Logic circuit for Problem 3.20

---

**Solution:**

### [Textbook 3.23] Schematic from Equation, I

Draw a schematic for the following unsimplified logic equation:  $f(x, y, z) = (\bar{x} \wedge y \wedge \bar{z}) \vee (\bar{x} \wedge \bar{y} \wedge \bar{z}) \vee (x \wedge \bar{y} \wedge \bar{z})$ .

---

**Solution:**

### [Textbook 6.11] Non-Unique Cover

Design a 4-input circuit to implement Equation 1:

$$f = \sum m(0, 1, 2, 9, 10, 11) \quad (1)$$

---

**Solution:**

## [Textbook 6.14] Seven-Segment Decoder, I

The next few problems share the description of a seven-segment decoder, a combinational circuit with a four-bit input  $a$  and a seven-bit output  $q$ . Each bit of  $q$  corresponds to one of the seven segments of a display, as shown in Figure 2. That is, bit 0 (LSB) corresponds to the middle segment, bit 1 the upper left segment, and so on, with bit 6 (MSB) controlling the top segment. A full decoder decodes all 16 input combinations - approximating letters A-F (capital A, C, E, F and lowercase b, d) for combinations 10 – 15. A decimal decoder decodes only combinations 0 – 9, the remainder are don't cares.

 


Figure 2: 7-segment Display

Design a sum-of-products circuit for segment 0 of a full seven-segment decoder.

---

**Solution:**

## [Textbook 6.15] Seven-Segment, II

Design a sum-of-products circuit for segment 1 of the full seven-segment decoder

---

**Solution:**

## [Textbook 6.21] Decimal Seven-Segment, I

Design a sum-of-products circuit for segment 0 of a decimal seven segment decoder

---

**Solution:**

## **[Textbook 6.28] Product-of-sums Seven-Segment, II**

Design a product-of-sums circuit for segment 0 of the full seven segment decoder.

---

**Solution:**

## **[Textbook 6.46] Adder Karnaugh Maps, I**

A half adder is a circuit that takes in one-bit binary numbers  $a$  and  $b$  and outputs a sum  $s$  and a carry out  $co$ . The concatenation of  $co$  and  $s$ ,  $co, s$  is the two-bit value that results from adding  $a$  and  $b$  (e.g., if  $a = 1$  and  $b = 1$ ,  $s = 0$  and  $co = 1$ )

- Write out the truth tables for the  $s$  and  $co$  outputs of a half adder
- Draw Karnaugh maps for the  $s$  and  $co$  outputs of the half adder
- Circle the prime implicants and write out the logic equations for the  $s$  and  $co$  outputs of the half adder.

---

**Solution:**

## [Textbook 8.5] Building Large Decoders.

Implement a  $6 \rightarrow 64$  using  $3 \rightarrow 8$  decoders as building blocks. Show the logic for outputs  $b_{63}$ ,  $b_{48}$ ,  $b_{17}$  and  $b_{11}$

---

**Solution:**

## [Example] Building Large Encoders.

Build a  $16 \rightarrow 4$  Encoder from  $4 \rightarrow 2$  Encoders.

---

**Solution:**